

Synthesizing your Processor

Pooria M. Yaghini

Performance Metrics

- Execution time
- MIPS (Million Instruction per Second)
- Operational Clock Frequency

Performance Metrics

- **Execution time**
- MIPS (Million Instruction per Second)
- Operational Clock Frequency

Performance Metrics

$$\text{Execution time} = \# \text{Inst.} * \text{CPI} * (1 / \text{Freq.})$$

Notes:

- In a Single-cycle processor, CPI equals to 1.
 - So frequency is the only factor to make it faster


Performance Metrics

$$\text{Execution time} = \# \text{Inst.} * \text{CPI} * (1 / \text{Freq.})$$


Notes:

- In a Single-cycle processor, CPI equals to 1.
 - So frequency is the only factor to make it faster
- What is your suggestion to improve the frequency?


Single-cycle Architecture

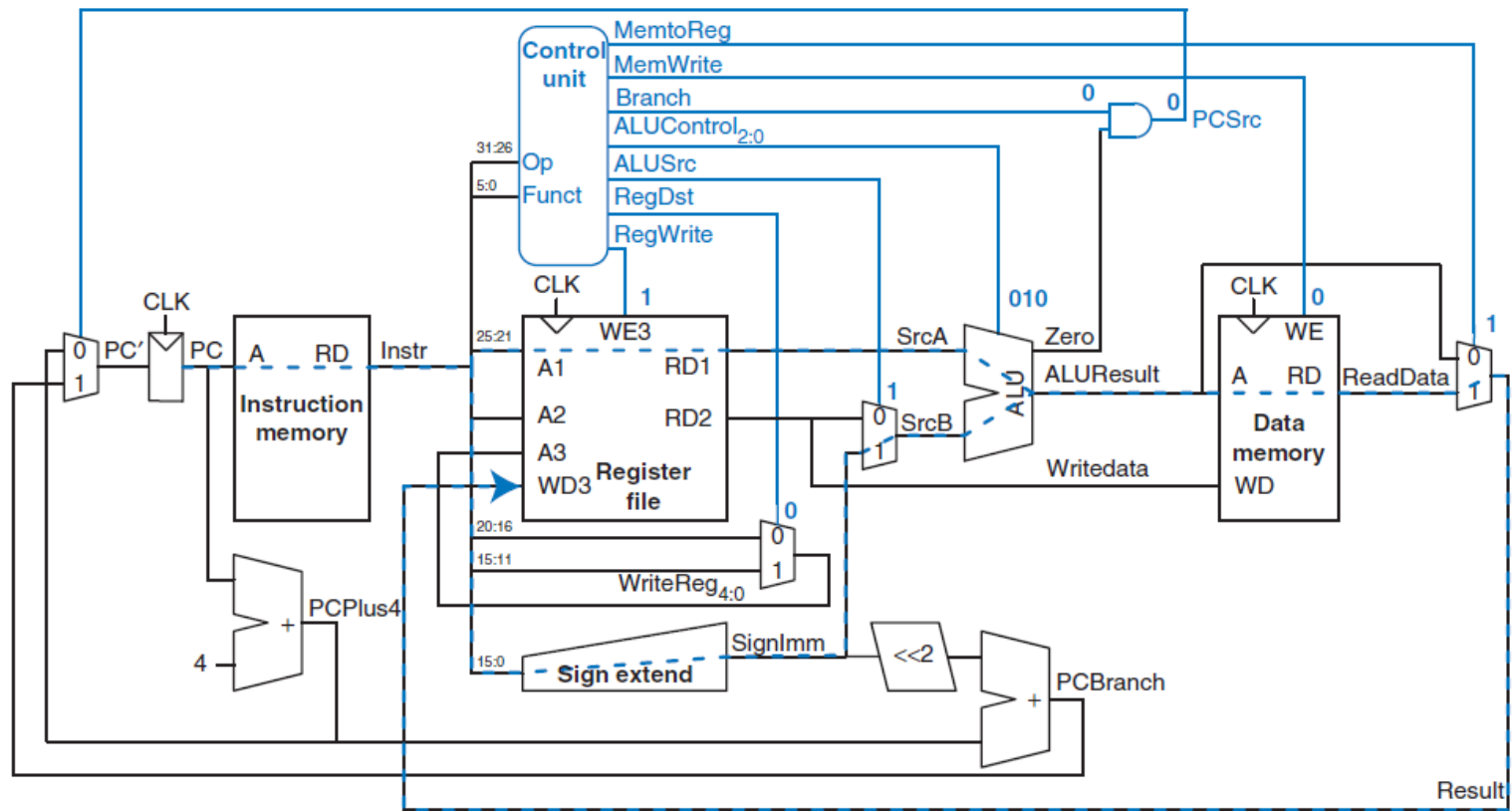

Multicycle Architecture

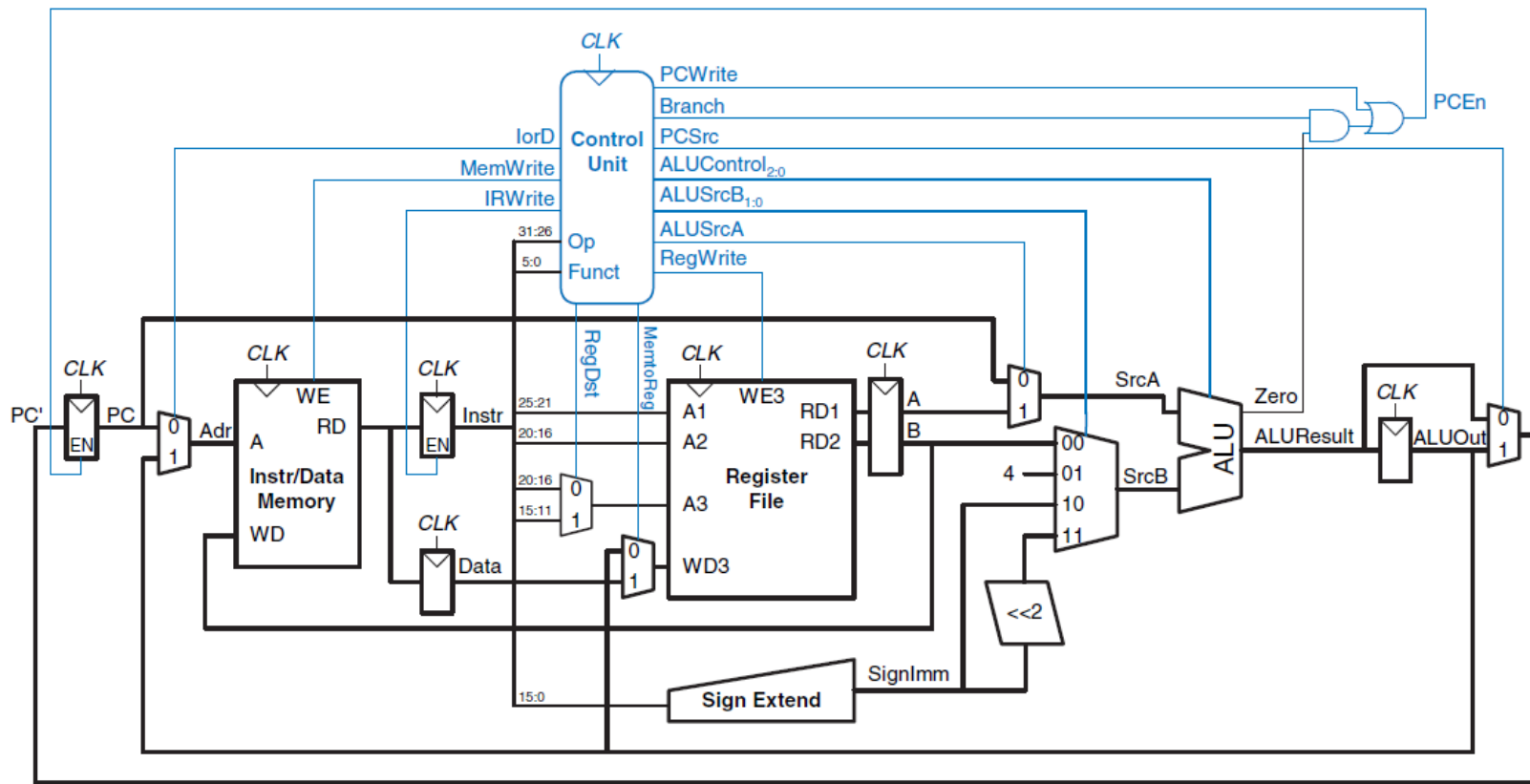

Multicycle Architecture

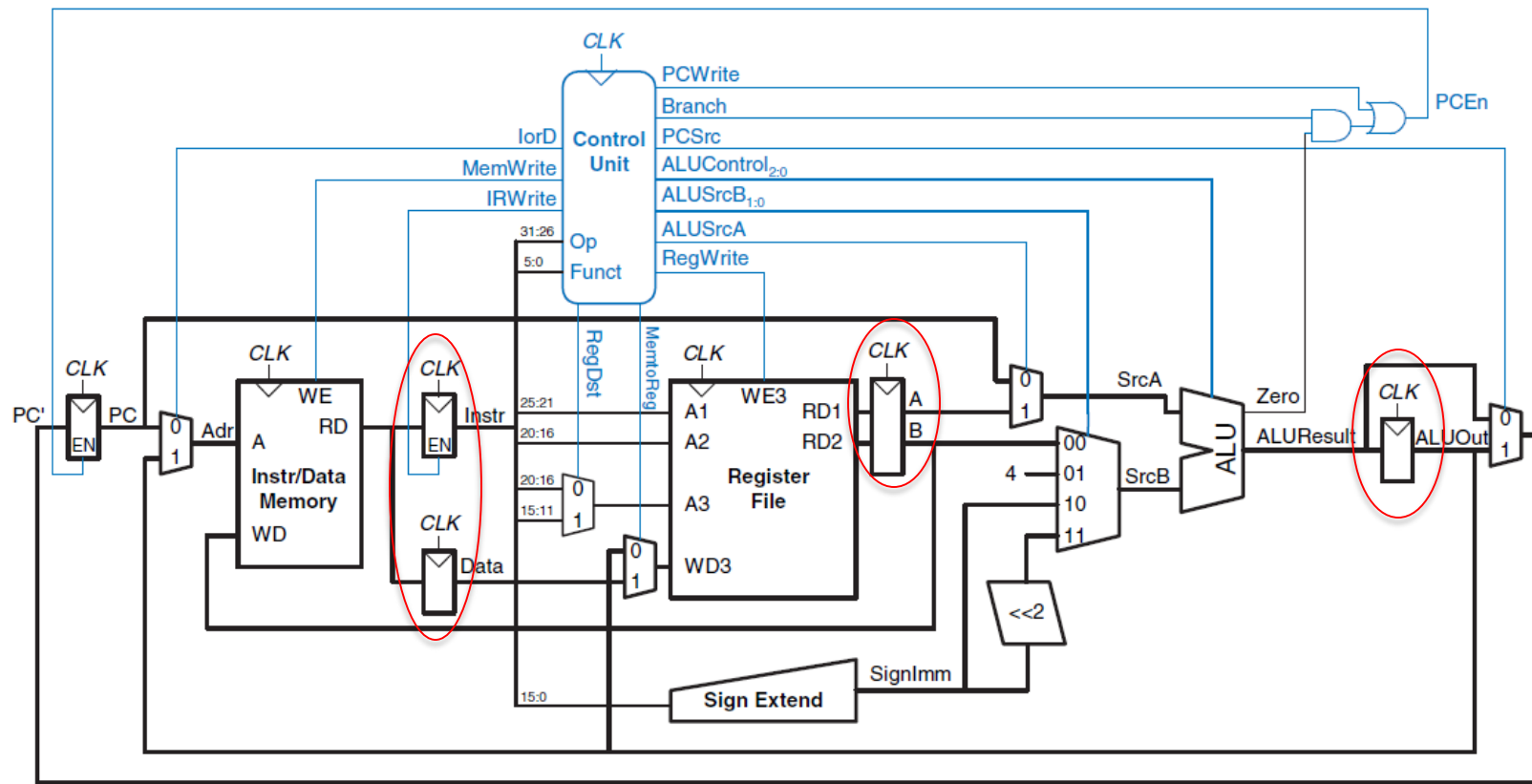

Performance Evaluation


The SPECINT2000 benchmark consists of approximately 25% loads, 10% stores, 11% branches, 2% jumps, and 52% Data Processing instructions. Determine the average CPI for this benchmark.


Performance Evaluation

Now you have achieved building a single-cycle ARM processor in a 28nm CMOS manufacturing process.

- First, determine the delay for each major module of your design. Then compute the execution time for a program with 100 billion instructions.
- Second, do the same for the multicycle processor and compare.
 - If you have not implemented the multicycle processor, consider the following equation to determine the clock period:
 - $T_c = t_{pcq} + t_{mux} + \text{maximum}(t_{ALU} + t_{mux}, t_{mem}) + t_{setup}$

Synthesis Flow

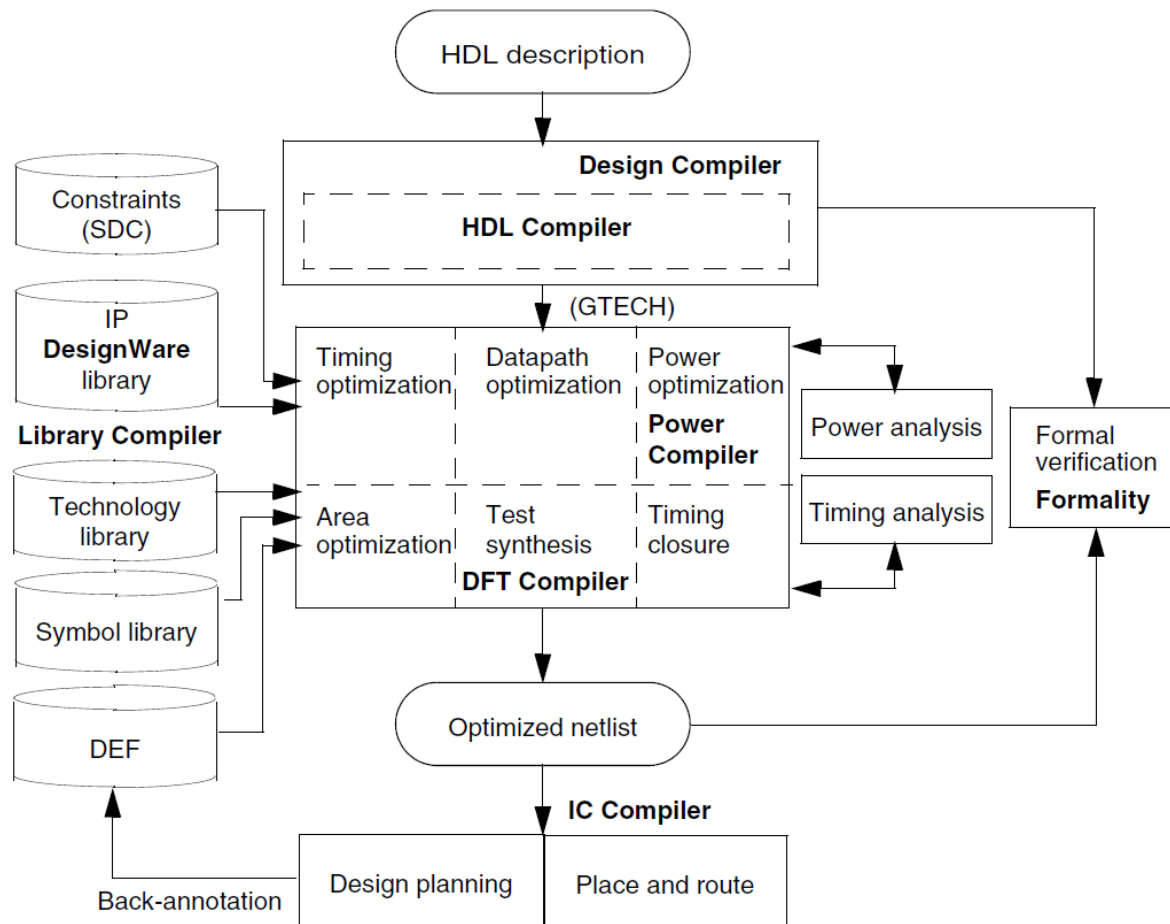

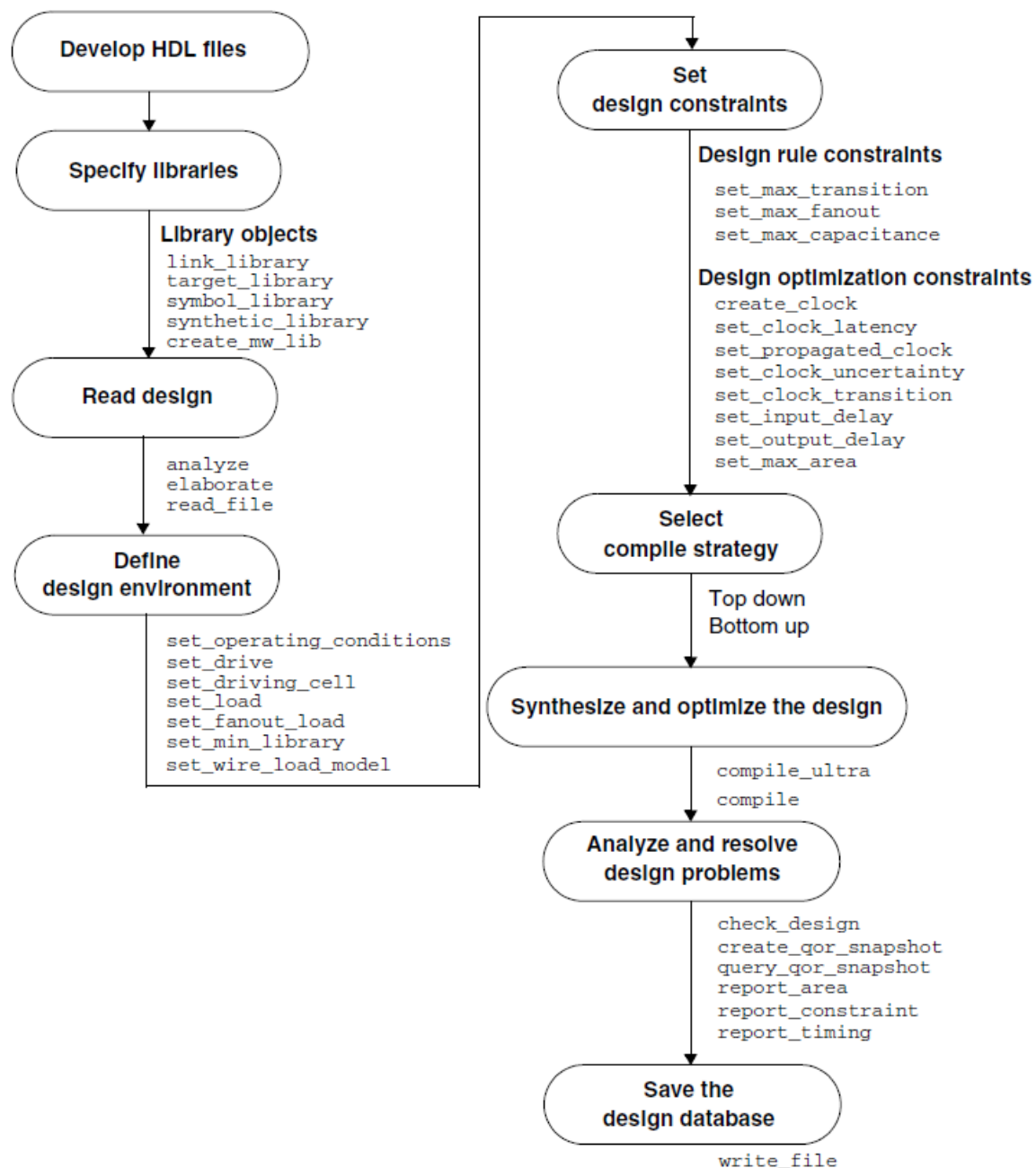

Synthesis Commands

- analyze
- elaborate
- compile[_ultra]
- report_
 - area [-hierarchy]
 - power
 - timing

Synthesis Commands

- **set_max_area**

- Sets the max_area attribute to a specified value on the current design. This command is only supported in DC Expert with the **compile** command. If you specify a max_area value and run the **compile_ultra** command, the max_area value is ignored and the default (zero) is used.

```
dc_shell> set_max_area 0.0
```

Synthesis Commands

- **set_max_delay**

- Specifies a maximum delay target for paths in the current design.

The following example shows how to optimize the design so that any delay path to a port named Y is less than 10 units.

```
dc_shell> set_max_delay 10.0 -to {Y}
```

This example shows how to specify that all paths from cell ff1a or ff1b that pass through cell u1 and end at cell ff2e must be less than 15.0 units.


```
dc_shell> set_max_delay 15.0 -from {ff1a ff1b} -through {u1} -to {ff2e}
```

Synthesis Commands


- **More commands to help optimization**

```
dc_shell> set_max_leakage_power 0
```



Process of Synthesis

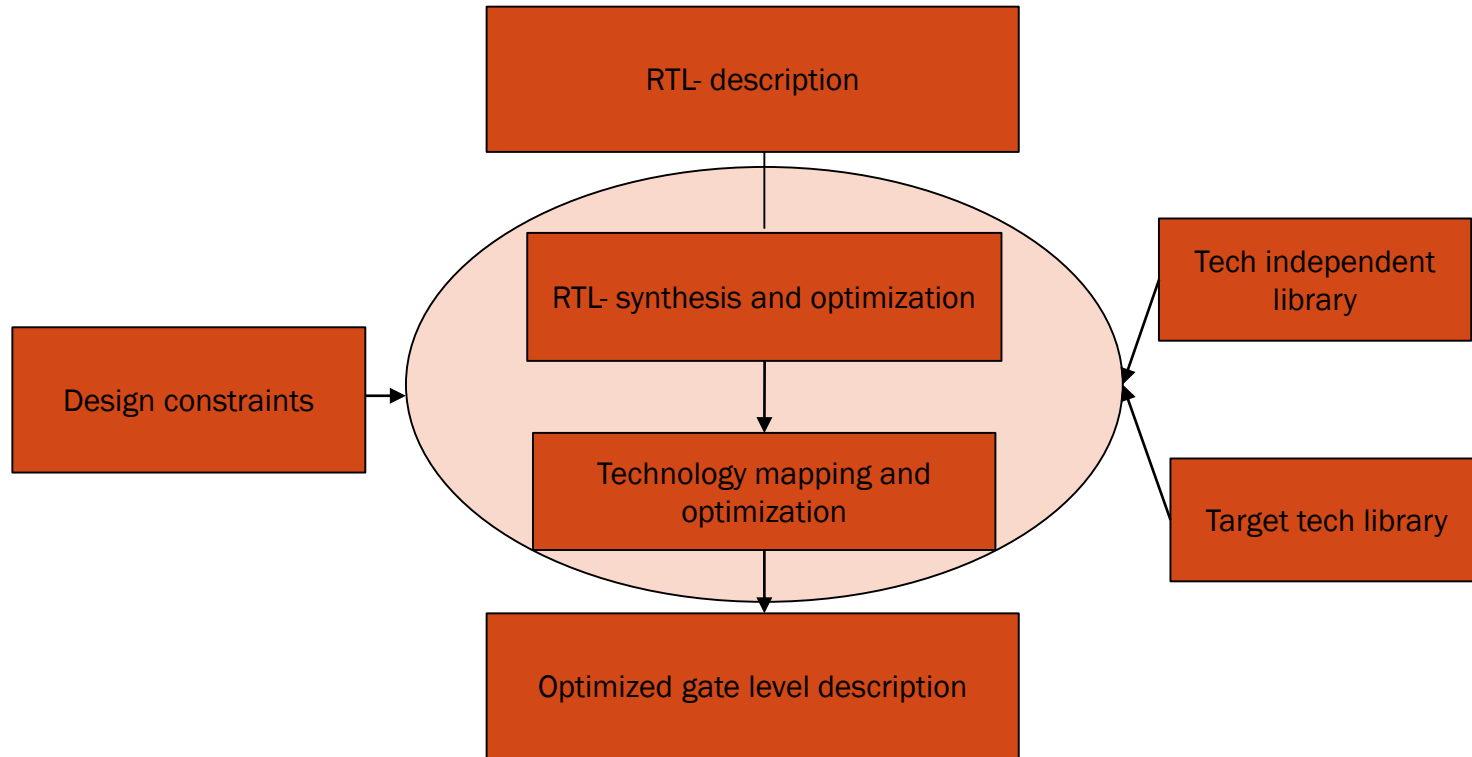


Steps of Synthesis

 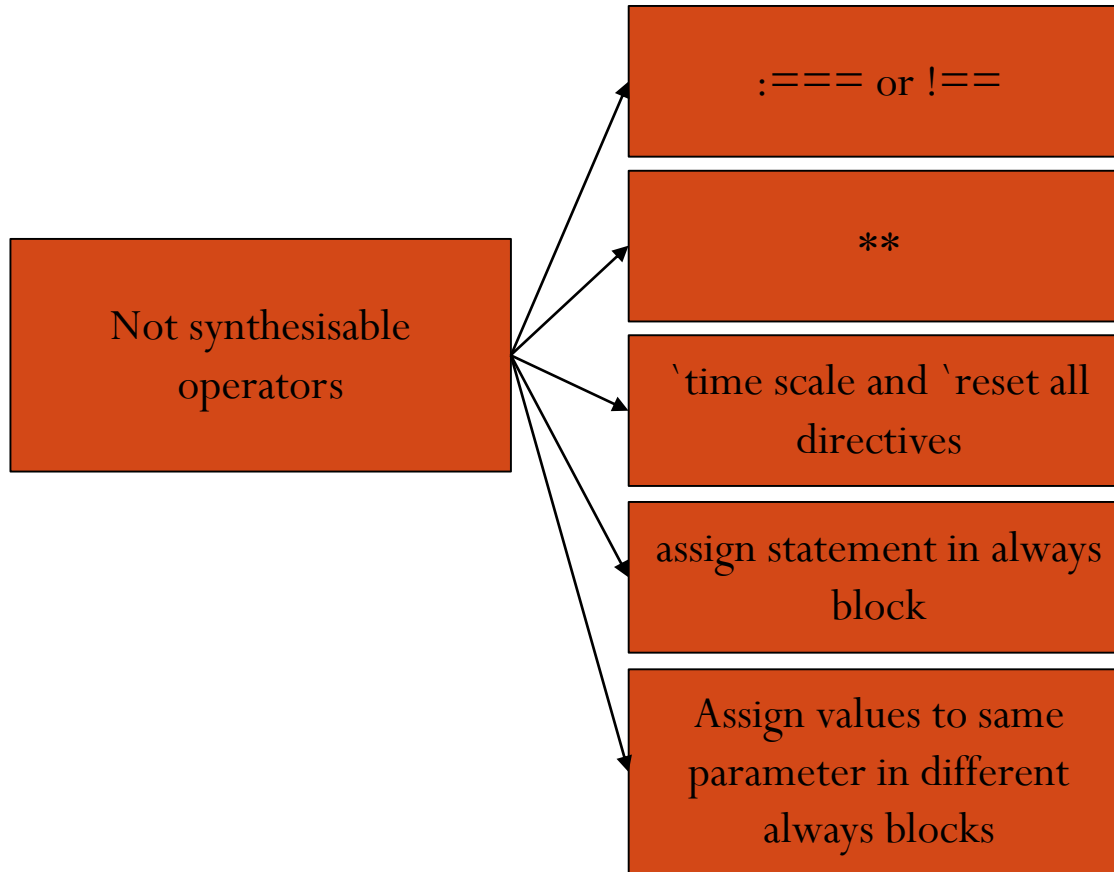


Not Synthesisable Operators



Optimization Methods in Design Compiler

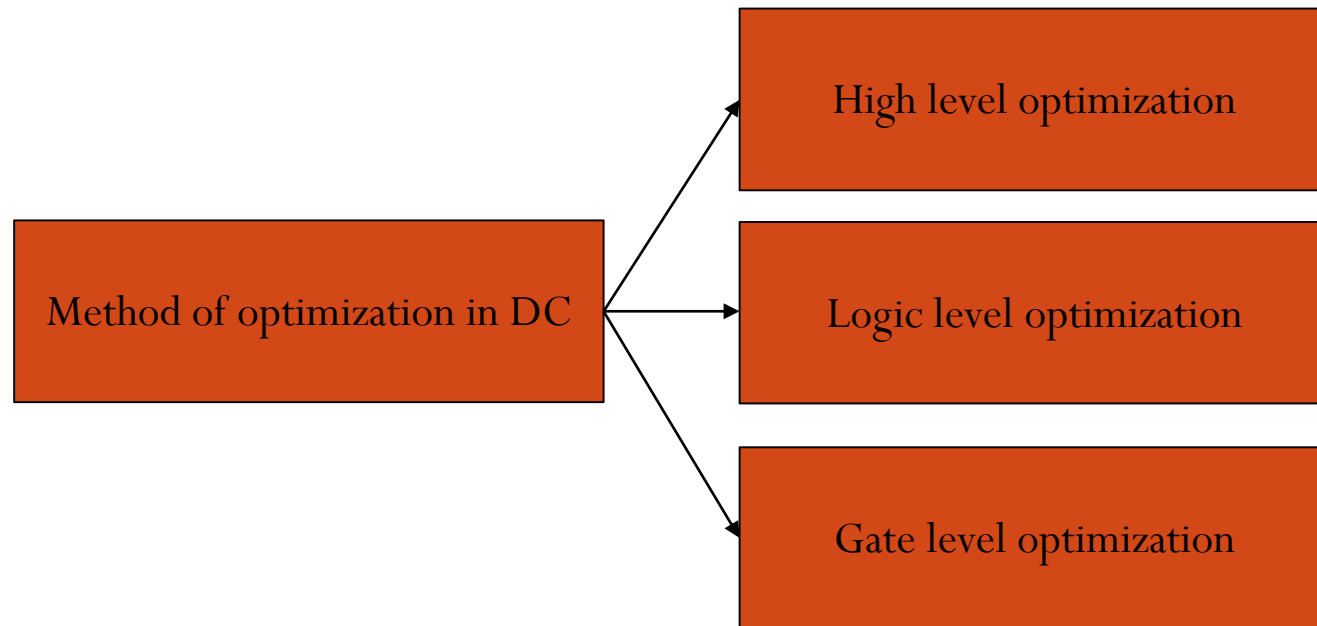


High Level Optimization

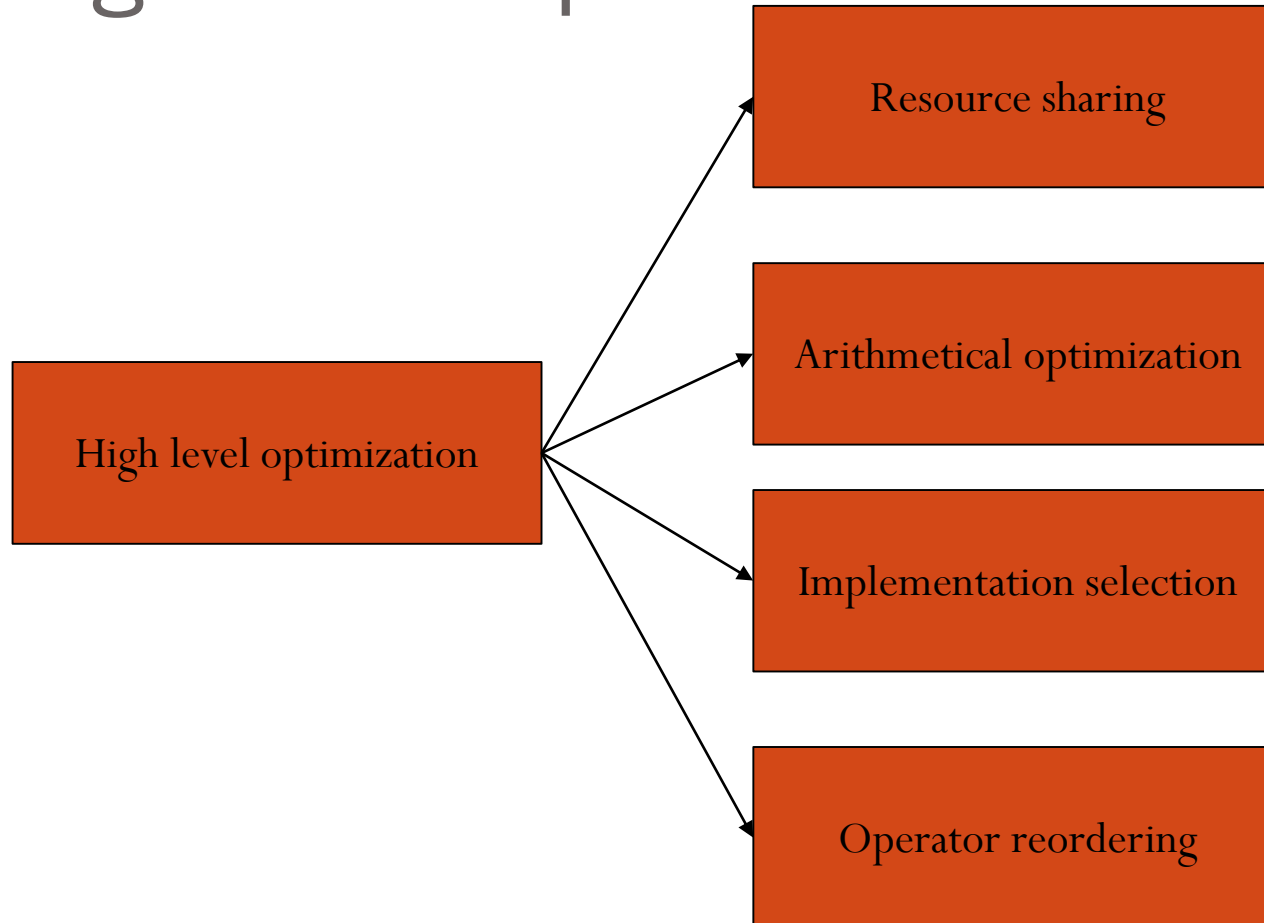



Resource Sharing
 
```
if (sel==2'b00)
    y=a+b;
else if (sel==2'b01)
    y=c+d;
else if (sel==2'b10)
    y=e+f;
else y=g+h;
....
```




Arithmetical Optimization

- $Z1 = A + B + C$
- $Z2 = C + D + B$

 
 


Implementation Selection



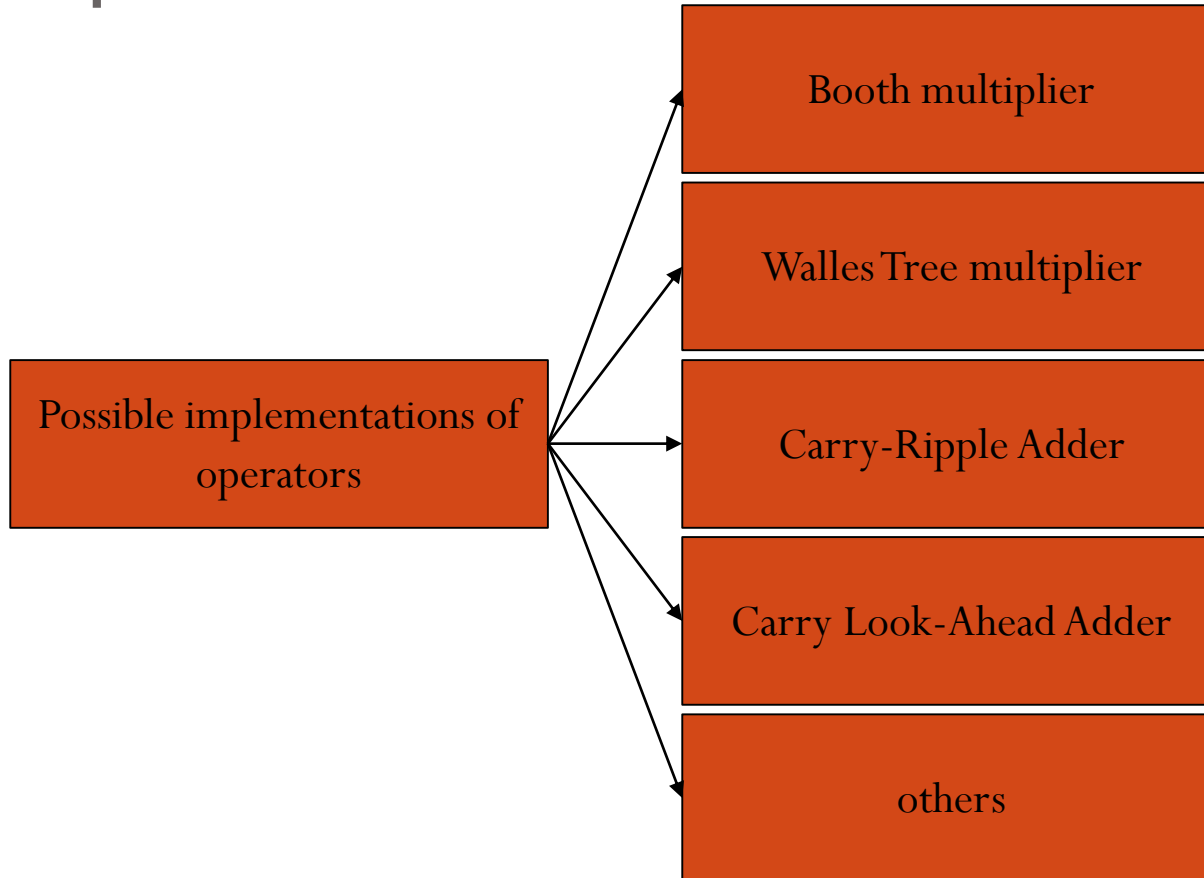


Operator Reordering


$$Y = a * b + e + f + g$$

  

Gate Level Optimization

   

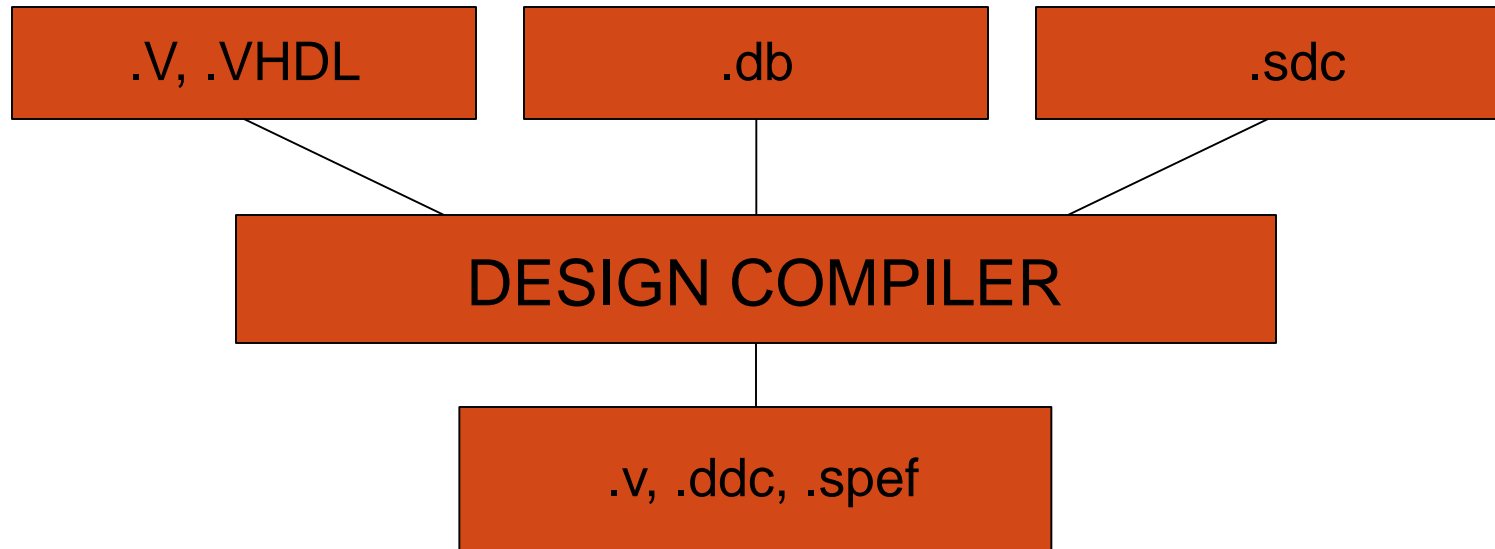
Inputs and Output of Logic Synthesis Tool (DC)



Behavioral Verilog Code of EFF

```
module E_ff(q, data, enable,  
reset, clock);  
output q;  
input data, enable, reset,  
clock;  
reg q;  
always @(posedge clock) //  
whenever the clock makes a  
transition to 1  
if (reset == 0)  
q = 1'b0;  
else if (enable==1)  
q = data;  
else q = q  
endmodule
```

Synthesized Design View of EFF from DC

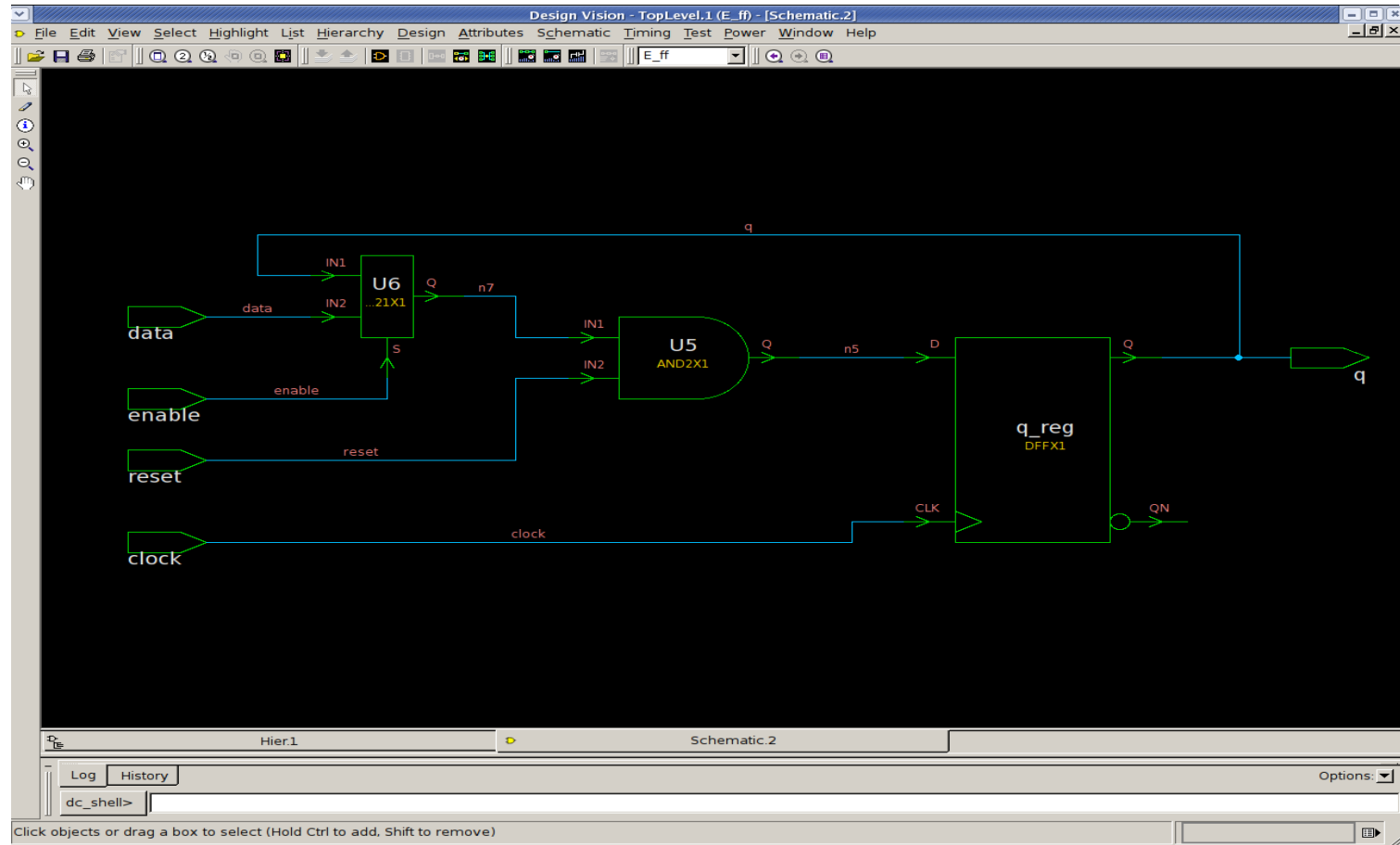

Gate Level Verilog from DC

```
module E_ff ( q, data, enable, reset, clock );  
    input data, enable, reset, clock;  
    output q;  
    wire    n5, n6;  
  
    DFFX1 q_reg ( .D(n5), .CLK(clock), .Q(q) );  
    AND2X1 U5 ( .IN1(n6), .IN2(reset), .Q(n5) );  
    MUX21X1 U6 ( .IN1(q), .IN2(data),  
    .S(enable), .Q(n6) );  
endmodule
```

SRAM

```
module dmem( input  logic      clk, we,
             input  logic [31:0] a,  wd,
             output logic [31:0] rd);

`ifdef sim
    logic [31:0] RAM[63:0];

    assign rd = RAM[a[31:2]]; // word aligned

    always @( posedge clk )
        if (we)
            RAM[ a[31:2] ] <= wd;
`else

    SRAM1RW512x32 RAM (
                                .A    ( a[8:0] ),
                                .CE    ( 1'b1   ),
                                .WEB   ( ~we    ),
                                .OEB   ( we     ),
                                .CSB   ( 1'b0   ),
                                .I     ( wd     ),
                                .O     ( rd     )
                                );
`endif
endmodule
```