

# EECS 31L: Introduction to Digital Design Lab Lecture 4

---

Pooria M.Yaghini

The Henry Samueli School of Engineering  
Electrical Engineering and Computer Science  
University of California, Irvine

# Lecture 4: Outline



---

- Sequential Coding
- If, case, for, while, ...
- Storage Elements
  
# Lecture 4: Combinational vs Sequential logic


---

- By definition, combinational logic is that in which the output of the circuit depends solely on the current inputs. It is then clear that, in principle, the system requires no memory and can be implemented using conventional logic gates.
- In contrast, **sequential** logic is defined as that in which the output does depend on previous inputs. Therefore, storage elements are required, which are connected to the combinational logic block through a feedback loop, such that now the stored states (created by previous inputs) will also affect the output of the circuit.




# Lecture 4: Sequential Coding

- **Sequential Circuits**
  - D Latch




 


E	D	Q	$\overline{Q}$
0	0	latch	latch
0	1	latch	latch
1	0	0	1
1	1	1	0

 

# Lecture 4: Sequential Coding

- Sequential Circuits
  - D Flip-Flop

  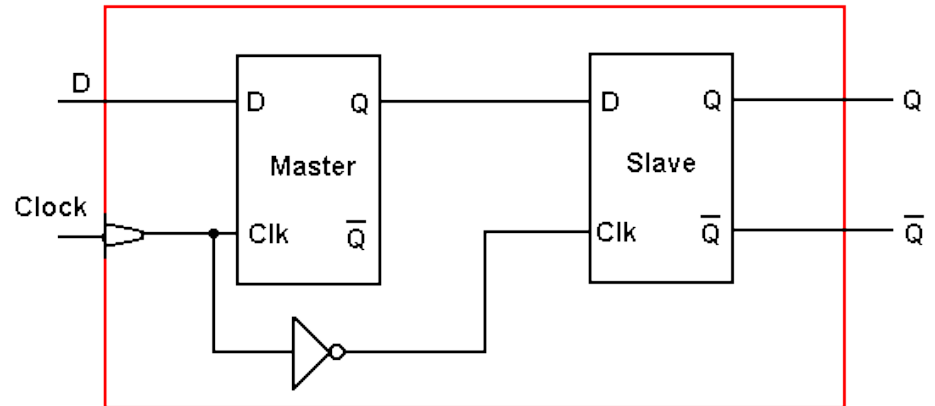 

# Lecture 4: Sequential Coding

---

## Structured procedures

- **initial** procedure
- **always** procedure
  - always
  - always\_comb
  - always\_latch
  - always\_ff
- **final** procedure
- **task**
- **function**

# Lecture 4: Sequential Coding

---

- **initial**
  - is enabled **only once** at the **beginning** of a simulation
  - Not synthesizable
- **always**
  - is enabled at the beginning of a simulation
  - execute **repeatedly** until the simulation is terminated
- **final**
  - is enabled at the **end** of simulation time and execute **only once**
  - Not synthesizable

# Lecture 4: Sequential Coding

---

There are four forms of always procedures

- **always**
  - represents a general purpose always procedure, which can be used to represent repetitive behavior such as clock oscillators. The construct can also be used with proper timing controls to represent combinational, latched, and sequential hardware behavior.
  - If an always procedure has no control for simulation time to advance, it will create a simulation deadlock condition.
- **always\_comb**
  - For modeling combinational logic
- **always\_latch**
  - for modeling latched logic behavior
- **always\_ff**
  - can be used to model synthesizable sequential logic behavior
  - imposes the restriction that it contains one and only one event control and no blocking timing controls.
  - Variables on the left-hand side of assignments within an always\_ff procedure, including variables from the contents of a called function, shall not be written to by any other process.



# Lecture 4: Sequential Coding

---

```
always clock = ~clock;          /* Deadlock Example */  
  
always #10 clock = ~clock;      /* Correct Example */
```

```
                                /* Latch Example */  
always_latch  
    if( en ) q <= d;
```

```
                                /* Flip Flop Example */  
always_ff @(posedge clock)  
    q <= d;
```

# Lecture 4: Sequential Coding

---

- **Sensitivity list**

A list of signals a process is sensitive to.

- The sensitivity list is a compact way of specifying the set of signals, events on which may resume a process. A sensitivity list is specified right after the keyword **always** or **always\_ff**.
- Upon initialization, all always blocks are executed once
- After that, always blocks are executed in a data-driven manner, they are activated by events on signals in the sensitivity list.
- The always keyword must be followed by an edge-sensitive event control (the @ token).
- The sensitivity list of the event control cannot contain **posedge** or **negedge** qualifiers.


# Lecture 4: Sequential Coding

---

- **Sensitivity list**

A list of signals a process is sensitive to.

 - The sensitivity list is a compact way of specifying the set of signals, events on which may resume a process. A sensitivity list is specified right after the keyword **always** or **always\_ff**.
- Upon initialization, all always blocks are executed once
- After that, always blocks are executed in a data-driven manner, they are activated by events on signals in the sensitivity list.




# Lecture 4: Sequential Coding

- **Sensitivity list**

A list of signals a process is sensitive to.

- The sensitivity list is a compact way of specifying the set of signals, events on which may resume a process. A sensitivity list is specified right after the keyword **always** or **always\_ff**.
- Upon initialization, all always blocks are executed once
- After that, always blocks are executed in a data-driven manner, they are activated by events on signals in the sensitivity list.

When does the output **q** change?

 

# Lecture 4: Sequential Coding


- **Sensitivity list**

A list of signals a process is sensitive to.

- The sensitivity list is a compact way of specifying the set of signals, events on which may resume a process. A sensitivity list is specified right after the keyword **always** or **always\_ff**.
- Upon initialization, all always blocks are executed once
- After that, always blocks are executed in a data-driven manner, they are activated by events on signals in the sensitivity list.

When does the output **q** change?

 If **clk** is triggered and **rst** is asserted or **d** value has changed.




# Lecture 4: Sequential Coding

- **Sensitivity list**

A list of signals a process is sensitive to.

- The sensitivity list is a compact way of specifying the set of signals, events on which may resume a process. A sensitivity list is specified right after the keyword **always** or **always\_ff**.
- Upon initialization, all always blocks are executed once
- After that, always blocks are executed in a data-driven manner, they are activated by events on signals in the sensitivity list.
 
```
always_ff
begin
    if ( rst == 1'b1) begin
        q <= 1'b0;
    end else begin
        q <= d;
    end
end
```



# Lecture 4: Sequential Coding


- **Sensitivity list**

A list of signals a process is sensitive to.

- The sensitivity list is a compact way of specifying the set of signals, events on which may resume a process. A sensitivity list is specified right after the keyword **always** or **always\_ff**.
- Upon initialization, all always blocks are executed once
- After that, always blocks are executed in a data-driven manner, they are activated by events on signals in the sensitivity list.

When does the following code should run to model a flip-flop?
 
```
always_ff
begin
    if ( rst == 1'b1) begin
        q <= 1'b0;
    end else begin
        q <= d;
    end
end
```



# Lecture 4: Sequential Coding

- **Sensitivity list**


A list of signals a process is sensitive to.

- The sensitivity list is a compact way of specifying the set of signals, events on which may resume a process. A sensitivity list is specified right after the keyword **always** or **always\_ff**.
- Upon initialization, all always blocks are executed once
- After that, always blocks are executed in a data-driven manner, they are activated by events on signals in the sensitivity list.

When does the following code should run to model a flip-flop?

→ If **clk** is triggered and **rst** is asserted or **d** value has changed.
 
```
always_ff
begin
    if ( rst == 1'b1) begin
        q <= 1'b0;
    end else begin
        q <= d;
    end
end
```





# Lecture 4: Sequential Coding

- **Sensitivity list**


A list of signals a process is sensitive to.

- The sensitivity list is a compact way of specifying the set of signals, events on which may resume a process. A sensitivity list is specified right after the keyword **always** or **always\_ff**.
- Upon initialization, all always blocks are executed once
- After that, always blocks are executed in a data-driven manner, they are activated by events on signals in the sensitivity list.

When does the following code should run to model a flip-flop?

→ So the always block should be sensitive to **clk** signal.
 
```
always_ff @(posedge clk)
begin
    if ( rst == 1'b1) begin
        q <= 1'b0;
    end else begin
        q <= d;
    end
end
```



# Lecture 4: Blocking vs Non-blocking Assignment

## Assignment statements

```
/* Example blocking vs non-blocking */  
  
module nonblock1;  
    logic a, b, c, d, e, f;  
  
    // blocking assignments  
    initial begin  
        a = #10 1; // a will be assigned 1 at time 10  
        b = #2 0;  // b will be assigned 0 at time 12  
        c = #4 1;  // c will be assigned 1 at time 16  
    end  
  
    // nonblocking assignments  
    initial begin  
        d <= #10 1; // d will be assigned 1 at time 10  
        e <= #2 0;  // e will be assigned 0 at time 2  
        f <= #4 1;  // f will be assigned 1 at time 4  
    end  
  
endmodule
```

*scheduled  
changes at  
time 2*

**e = 0**

*scheduled  
changes at  
time 4*


**f = 1**

*scheduled  
changes at  
time 10*

**d = 1**
 
# Lecture 4: Storage Elements

- Latch
  - Positive-Level D Latch with asynchronous reset
  - Negative-Level D Latch with asynchronous reset
- Flip-Flop
  - Positive-Edge D Flip-Flop with synchronous reset
  - Negative-Edge D Flip-Flop with synchronous reset
  - Positive-Edge D Flip-Flop with asynchronous reset
  - Negative-Edge D Flip-Flop with asynchronous reset



# Lecture 4: Storage Elements



---

- **Clock**





# Lecture 4: Storage Elements

- Clock

  



# Lecture 4: Storage Elements

- Clock

  



# Lecture 4: Storage Elements

- **Clock**

  

# Lecture 4: Storage Elements



- **Clock**

  





# Lecture 4: Storage Elements

- Clock

  



# Lecture 4: Storage Elements

- Clock

  



# Lecture 4: Storage Elements

- **Clock**

  


# Lecture 4: Storage Elements

- **Clock**

  


# Lecture 4: Storage Elements

- Clock

 


Is there anything wrong?

 
 
# Lecture 4: Storage Elements

- Latch
  - Positive-Level D Latch with asynchronous reset


```
module PDL ( input d, input en, input rst;  
             output logic q);  
  
    always( ? , ? ) begin  
        if (? == '?1')  
            ? <= '?';  
        else if(? == '?')  
            ? <= ?;  
    end  
  
endmodule
```


 
# Lecture 4: Storage Elements

- Latch
  - Positive-Level D Latch with asynchronous reset

```
module PDL ( input d, input en, input rst;  
             output logic q );  
  
    always( rst , en ) begin  
        if ( rst == 1'b1 )  
            q <= 1'b0;  
        else if( en == 1'b1 )  
            q <= d;  
    end  
  
endmodule
```



# Lecture 4: Storage Elements


- Latch
  - Positive-Level D Latch with asynchronous reset

```
module PDL ( input d, input en, input rst;
             output logic q);

    always( rst , en ) begin
        if ( rst == 1'b1)
            q <= 1'b0;
        else if( en == 1'b1 )
            q <= d;

    end

endmodule
```

 

Is this  
implementation  
exact and correct?



# Lecture 4: Storage Elements


- Latch
  - Positive-Level D Latch with asynchronous reset

```
module PDL ( input d, input en, input rst;
             output logic q);

    always( rst , en ) begin
        if ( rst == 1'b1)
            q <= 1'b0;
        else if( en == 1'b1 )
            q <= d;

    end

endmodule
```

 


Is this  
implementation  
exact and correct?  
NO !!!  
What if **en** is 1'b1  
and value of **d**  
changes?
 
# Lecture 4: Storage Elements

- Latch
  - Positive-Level D Latch with asynchronous reset

```
module PDL ( input d, input en, input rst;  
             output logic q );  
  
    always( rst , en, d ) begin  
        if ( rst == 1'b1 )  
            q <= 1'b0;  
        else if( en == 1'b1 )  
            q <= d;  
    end  
  
endmodule
```




Add the **d** to the sensitivity list.
 
# Lecture 4: Storage Elements

- Latch
  - Positive-Level D Latch with asynchronous reset

```
module PDL ( input d, input en, input rst;  
             output logic q);  
  
    always_latch begin  
        if ( rst == 1'b1)  
            q <= 1'b0;  
        else if( en == 1'b1 )  
            q <= d;  
    end  
  
endmodule
```




Or use `always_latch`
 
# Lecture 4: Storage Elements

- Latch
  - Negative-Level D Latch with asynchronous reset


```
module PDL ( input d, input en, input rst;  
             output logic q);  
  
    always_latch begin  
        if ( rst == 1'b1)  
            q <= 1'b0;  
        else if( en == 1'b0 )  
            q <= d;  
    end  
  
endmodule
```


 
# Lecture 4: Storage Elements

- Flip-Flop
  - Positive-Edge D Flip-Flop with synchronous reset


```
module PDFF ( input d, input clk, input rst;  
              output logic q );  
  
    always_ff @( posedge clk ) begin  
  
        if ( rst == 1'b1 ) begin  
            q <= 1'b0;  
        end else begin  
            q <= d;  
        end  
  
    end  
  
endmodule
```


 
# Lecture 4: Storage Elements

- Flip-Flop
  - Negative-Edge D Flip-Flop with synchronous reset


```
module NDDFF( input d, input clk, input rst;  
              output logic q);  
  
    always_ff @( negedge clk ) begin  
  
        if ( rst == 1'b1) begin  
            q <= 1'b0;  
        end else begin  
            q <= d;  
        end  
  
    end  
  
endmodule
```


 
# Lecture 4: Storage Elements

- Flip-Flop
  - Positive-Edge D Flip-Flop with asynchronous reset


```
module PDFF ( input d, input clk, input rst;  
              output logic q );  
  
    always_ff @( posedge clk, rst ) begin  
  
        if ( rst == 1'b1 ) begin  
            q <= 1'b0;  
        end else begin  
            q <= d;  
        end  
  
    end  
  
endmodule
```


 
# Lecture 4: Storage Elements

- Flip-Flop
  - Negative-Edge D Flip-Flop with asynchronous reset

```
module PDFF ( input d, input clk, input rst;  
              output logic q );  
  
    always_ff @( negedge clk, rst ) begin  
  
        if ( rst == 1'b1 ) begin  
            q <= 1'b0;  
        end else begin  
            q <= d;  
        end  
  
    end  
  
endmodule
```





# Lecture 4: Sequential Coding

---

- Purely sequential statements:
  - **if**
  - **case**
  - **for**

# Lecture 4: Sequential Coding

---

- **If statement**
  - The if statement is used to choose which statement should be executed depending on the conditional expression.


```
if (conditional expression) begin  
    statement1;  
    statement2;  
end else if (conditional expression)  
    statement3;  
else  
    statement4;
```

## Example

```
always_comb  
    if (a)  
        b = 4;  
    else if (d)  
        b = 5;  
    else  
        b = 1;
```

# Lecture 4: Sequential Coding

- **Example: 1-digit Decimal Counter**

 

```

module counter (
    input logic clk,
    output logic [3:0] count);


endmodule

```

# Lecture 4: Sequential Coding

 - Example: 1-digit Decimal Counter


```
module counter (  
    input logic clk,  
    output logic [3:0] count);  
  
    logic [3:0] temp;  
  
    always_ff @( posedge clk ) begin  
        if ( temp == 10 ) begin  
            temp <= 0;  
        end else begin  
            temp <= temp + 1;  
        end  
    end  
  
    assign count <= temp;  
  
endmodule
```



# Lecture 4: Sequential Coding

 - Example: 1-digit Decimal Counter


```
module counter (  
    input logic clk,  
    output logic [3:0] count);  
  
    logic [3:0] temp;  
  
    always_ff @( posedge clk ) begin  
        if ( temp == 10 ) begin  
            temp <= 0;  
        end else begin  
            temp <= temp + 1;  
        end  
    end  
  
    assign count <= temp;  
  
endmodule
```



What happens if  
temp value is not  
zero?

# Lecture 4: Sequential Coding

- Example: 1-digit Decimal Counter

 

```
module counter (  
    input logic clk,  
    input logic reset,  
    output logic [3:0] count);  
  
    logic [3:0] temp;  
  
    always_ff @( posedge clk ) begin  
  
        if ( reset ) begin  
            temp <= 0;  
        end else begin  
            if ( temp == 10 ) begin  
                temp <= 0;  
            end else begin  
                temp <= temp + 1;  
            end  
        end  
    end  
  
    assign count <= temp;  
  
endmodule
```


What happens if  
temp value is not  
zero? It is better to  
reset the internal  
variables first

# Lecture 4: Sequential Coding

- Example: **Shift Register**

```
module shift_register
    #(N = 4); // number of stages
    ( input din, input clk, input rst;
      output dout);

endmodule
```

 

# Lecture 4: Sequential Coding

- Example: **Shift Register**

```
module shift_register
    #(N = 4); // number of stages
    ( input din, input clk, input rst;
      output dout);


    logic [0:N-1] q;

    always_ff @( posedge clk, rst ) begin

        if ( rst ) begin
            q <= { N {1'b0} };
        end else begin
            q <= { din , q[0:N-2] };
        end
    end

    assign dout = q[N-1];

endmodule
```

 



# Lecture 4: Sequential Coding

---

- **case Statement**

The case statement selects for execution one of several alternative sequences of statements; the alternative is chosen based on the value of the associated expression.

```
case ( expression )  
    expression : statement  
    expression {, expression} : statement  
    default : statement  
endcase
```

# Lecture 4: Sequential Coding

- **case Statement**

The case statement selects for execution one of several alternative sequences of statements; the alternative is chosen based on the value of the associated expression.

```
case ( expression )  
    expression : statement  
    expression {, expression} : statement  
    default : statement  
endcase
```

## Example

```
always_comb  
    case (opcode)  
        2'b00: y = a + b;  
        2'b01: y = a - b;  
        2'b10: y = a * b;  
        2'b11: y = a / b;  
    endcase
```

# Lecture 4: Sequential Coding

---

Which statement will be executed if  $a == 1'bZ$

```
logic a;  
case ( a )  
    1'b0 : statement1;  
    1'b1 : statement2;  
    1'bx : statement3;  
    1'bz : statement4;  
endcase
```

```
logic a;  
casez ( a )  
    1'b0 : statement1;  
    1'b1 : statement2;  
    1'bx : statement3;  
    1'bz : statement4;  
endcase
```

```
logic a;  
casex ( a )  
    1'b0 : statement1;  
    1'b1 : statement2;  
    1'bx : statement3;  
    1'bz : statement4;  
endcase
```

# Lecture 4: Sequential Coding

Which statement will be executed if  $a == 1'bZ$

```
logic a;  
case ( a )  
    1'b0 : statement1;  
    1'b1 : statement2;  
    1'bx : statement3;  
    1'bz : statement4;  
endcase
```

```
logic a;  
casez ( a )  
    1'b0 : statement1;  
    1'b1 : statement2;  
    1'bx : statement3;  
    1'bz : statement4;  
endcase
```

```
logic a;  
casex ( a )  
    1'b0 : statement1;  
    1'b1 : statement2;  
    1'bx : statement3;  
    1'bz : statement4;  
endcase
```

- The **casez** statement treats high-impedance (z) values as don't-care values and the **casex** statement treats high-impedance and unknown (x) values as don't care values. If any of the bits in the case expression or case item expression is a don't-care value then that bit position will be ignored.
- The don't-care value can be also specified by the question mark (?), which is equal to z value.

# Lecture 4: Sequential Coding

---

The case expression can be a constant expression.

```
logic a;  
case ( 1'b1 )  
  a : statement1;  
endcase
```

# Lecture 4: Sequential Coding

---

SystemVerilog provides special unique and priority modifiers to case, casex, and casez decisions. These modifiers are placed before the case, casex, or casez keywords:

NOTE—By specifying unique or priority, it is not necessary to code a default case to trap unexpected case values.

```
unique case (<case_expression>)  
    ... // case items  
endcase
```

```
priority case (<case_expression>)  
    ... // case items  
endcase
```

# Lecture 4: Sequential Coding

---

A unique case statement specifies that:

- ✓ Only one case select expression matches the case expression when it is evaluated
- ✓ One case select expression must match the case expression when it is evaluated

```
always_comb  
  unique case (opcode)  
    2'b00: y = a + b;  
    2'b01: y = a - b;  
    2'b10: y = a * b;  
    2'b11: y = a / b;  
  endcase
```

# Lecture 4: Sequential Coding

A **priority case** statement specifies that:

- ✓ At least one case select expression must match the case expression when it is evaluated
- ✓ If more than one case select expression matches the case expression when it is evaluated, the first matching branch must be taken

```
always_comb
  priority case (1'b1)
    irq0: irq = 4'b0001;
    irq1: irq = 4'b0010;
    irq2: irq = 4'b0100;
    irq3: irq = 4'b1000;
  endcase
```



# Lecture 4: Sequential Coding

---

## Looping Statements

Loop statements provide a means of modeling blocks of procedural statements.

- **forever**
  - continuously repeats the statement that follows it. Therefore, it should be used with procedural timing controls (otherwise it hangs the simulation).
- **repeat**
  - executes a given statement a fixed number of times. The number of executions is set by the expression, which follows the repeat keyword. If the expression evaluates to unknown, high-impedance, or a zero value, then no statement will be executed.
- **while**
  - executes a given statement until the expression is true. If a while statement starts with a false value, then no statement will be executed.
- **for**
  - executes a given statement until the expression is true. At the initial step, the first assignment will be executed. At the second step, the expression will be evaluated. If the expression evaluates to an unknown, high-impedance, or zero value, then the for statement will be terminated. Otherwise, the statement and second assignment will be executed. After that, the second step is repeated.

# Lecture 4: Sequential Coding

---

```
always begin  
    counter = 0;  
    forever #10 counter = counter + 1;  
end
```

```
initial begin  
    repeat (10) a = a + ~b;  
end
```

```
initial begin  
    for (index=0; index < 10; index = index + 2)  
        mem[index] = index;  
end
```

# Lecture 4: Sequential Coding

---


```
module test();  
    parameter MSB = 8;  
    logic [MSB-1:0] Vector;  
    integer t;  
  
    initial begin  
        t = 0;  
  
        while (t < MSB);  
            begin  
                //Initializes vector elements  
                Vector[t] = 1'b0;  
                t = t + 1;  
            end  
    end  
end
```

# Lecture 4: Sequential Coding
 
## Example: Ripple Carry Adder

$$s_j = a_j \text{ XOR } b_j \text{ XOR } c_j$$

$$c_{j+1} = (a_j \text{ AND } b_j) \text{ OR } (a_j \text{ AND } c_j) \text{ OR } (b_j \text{ AND } c_j)$$



```
module adder
  #(length = 8);
  ( input  [length-1] a, input [length-1] b, input cin,
    output [length-1] s, output cout);


endmodule
```

# Lecture 4: Sequential Coding
 
## Example: Ripple Carry Adder

$$s_j = a_j \text{ XOR } b_j \text{ XOR } c_j$$

$$c_{j+1} = (a_j \text{ AND } b_j) \text{ OR } (a_j \text{ AND } c_j) \text{ OR } (b_j \text{ AND } c_j)$$



```
module adder
#(length = 8);
  ( input  [length-1] a, input [length-1] b, input cin,
    output [length-1] s, output cout);


  always_comb begin
    logic [length:0] carry;
    carry[0] = cin;
    for ( int i=0; i< length; i= i + 1 ) begin
      s[i]      = a[i] ^ b[i] ^ carry[i];
      carry[i+1] = (a[i] & b[i]) | (a[i] & carry[i]) | (b[i] & carry[i]);
    end
    cout = carry[length];
  end
endmodule
```

# Lecture 4: Sequential Coding

- Example: **Barrel Shifter**

```
module barrel
    #(n = 8);
    (input  [n-1:0] inp,
     input          shift,
     output [n-1:0] outp );

endmodule
```

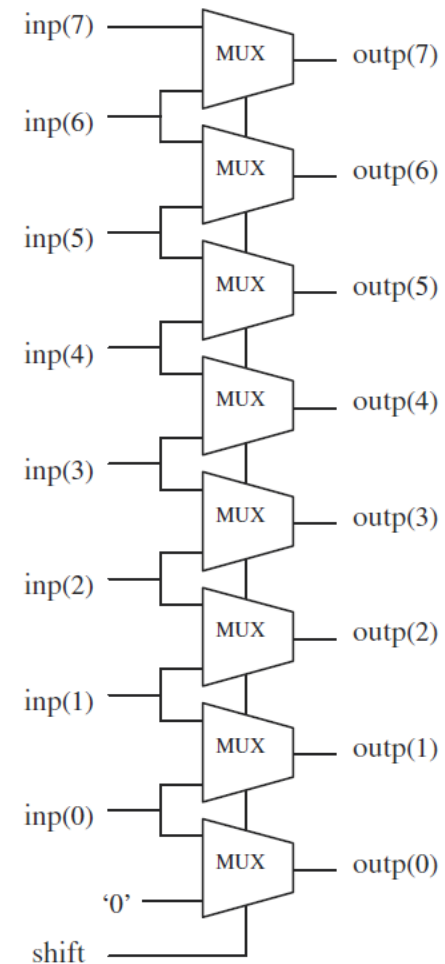

# Lecture 4: Sequential Coding

- Example: **Barrel Shifter**

```
module barrel
    #(n = 8);
    (input  [n-1:0] inp,
     input          shift,
     output [n-1:0] outp );

    always (inp, shift) begin
        if ( shift == 0)
            outp <= inp;
        else begin
            outp[0] <= 1'b0;
            for( int i=1; i<n; i++ ) begin
                outp[i] <= inp[i-1];
            end
        end
    end
endmodule
```

