

EECS 31L: Introduction to Digital Design Lab Lecture 6

Pooria M.Yaghini

The Henry Samueli School of Engineering
Electrical Engineering and Computer Science
University of California, Irvine

Lecture 6: Outline

- Finite State Machine

Lecture 6: Finite State Machine

Digital circuits can be classified as:

- Combinational
- Sequential

Lecture 6: Finite State Machine

Digital circuits can be classified as:

- Combinational
- Sequential

So what is “**finite state machine (FSM)**”?

- A third category?

Lecture 6: Finite State Machine

Digital circuits can be classified as:

- Combinational
- Sequential

So what is “**finite state machine (FSM)**”?

- A third category?
- No! Just a modeling (design) technique for sequential circuits

When is this technique recommended?

- For any sequential circuit?
- For certain sequential circuits?

Lecture 6: Finite State Machine

The FSM approach is recommended when:

Lecture 6: Finite State Machine

The FSM approach is recommended when:

- 1) The construction of a list with all system states is viable. (i.e., the states are well defined and the list is not too long)

Lecture 6: Finite State Machine

The FSM approach is recommended when:

- 1) The construction of a list with all system states is viable. (i.e., the states are well defined and the list is not too long)
- 2) All output values that must be produced by the system (in all states) are easily enumerable. The list must be the same in all states.

Lecture 6: Finite State Machine

The FSM approach is recommended when:

- 1) The construction of a list with all system states is viable. (i.e., the states are well defined and the list is not too long)
- 2) All output values that must be produced by the system (in all states) are easily enumerable. The list must be the same in all states.
- 3) All conditions for the machine to move from one state to another (in all states) are also easily enumerable.

Lecture 6: Finite State Machine

The FSM approach is recommended when:

- 1) The construction of a list with all system states is viable. (i.e., the states are well defined and the list is not too long)
- 2) All output values that must be produced by the system (in all states) are easily enumerable. The list must be the same in all states.
- 3) All conditions for the machine to move from one state to another (in all states) are also easily enumerable.

Lecture 6: Finite State Machine

The FSM approach is recommended when:

- 1) The construction of a list with all system states is viable. (i.e., the states are well defined and the list is not too long)
- 2) All output values that must be produced by the system (in all states) are easily enumerable. The list must be the same in all states.
- 3) All conditions for the machine to move from one state to another (in all states) are also easily enumerable.

Classical example: All sorts of controllers


- Traffic-light controller
- Elevator controller
- Control unit for microcontroller datapath

Lecture 6: Finite State Machine

FSM representations:

- From a specifications perspective: **State transition diagram**

State Transition Diagram

 


Lecture 6: Finite State Machine


FSM representations:

- From a specifications perspective: **State transition diagram**
- From a hardware perspective: **Sequential + combinational sections**

State Transition Diagram

 


Hardware

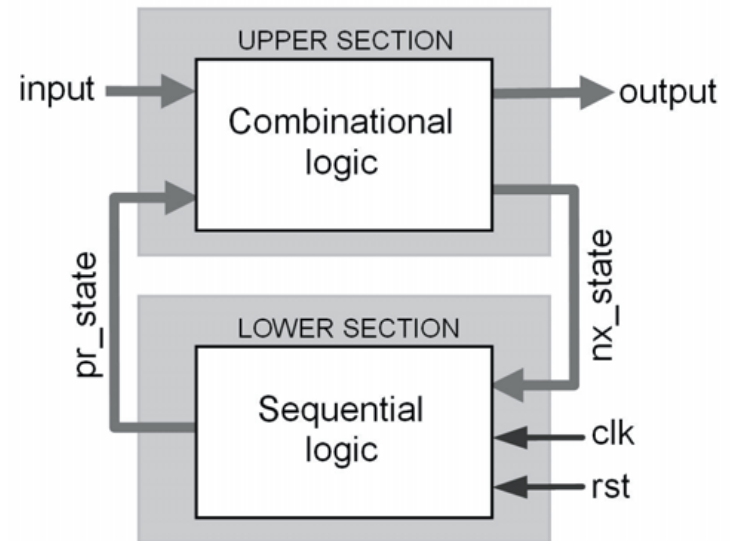

Lecture 6: Finite State Machine

Example: **String detector** (“mp3”)

 


Data input: **ascii_in**

Data output: **string_detected**

Operational inputs: **clk, rst**


Lecture 6: Finite State Machine

Example: **String detector** (“mp3”)

 


Lecture 6: Finite State Machine

Example: **String detector** ("mp3")

 

 State transition diagram
(4 states, Moore type)



Data input: **ascii_in**
Data output: **string_detected**
Operational inputs: **clk, rst**

Lecture 6: Finite State Machine

Manual design

Five-step design procedure:

Lecture 6: Finite State Machine

Manual design

Five-step design procedure:

Step 1: Draw state transition diagram.

Lecture 6: Finite State Machine

Manual design

Five-step design procedure:

Step 1: Draw state transition diagram.

Step 2: Write truth tables for `nx_state` and output.

Then rearrange truth tables replacing state names with corresponding binary values.

Lecture 6: Finite State Machine

Manual design

Five-step design procedure:

Step 1: Draw state transition diagram.

Step 2: Write truth tables for nx_state and output.

Then rearrange truth tables replacing state names with corresponding binary values.

Step 3: Get boolean expressions for nx_state and output.

Lecture 6: Finite State Machine

Manual design

Five-step design procedure:

Step 1: Draw state transition diagram.

Step 2: Write truth tables for nx_state and output.

Then rearrange truth tables replacing state names with corresponding binary values.

Step 3: Get boolean expressions for nx_state and output.

Step 4: Draw circuit, placing all flip-flops (D-type only) in the lower section and the combinational logic (for the expressions above) in the upper section.

Lecture 6: Finite State Machine

Manual design

Five-step design procedure:

Step 1: Draw state transition diagram.

Step 2: Write truth tables for nx_state and output.

Then rearrange truth tables replacing state names with corresponding binary values.

Step 3: Get boolean expressions for nx_state and output.

Step 4: Draw circuit, placing all flip-flops (D-type only) in the lower section and the combinational logic (for the expressions above) in the upper section.

Step 5 (optional): Add DFFs at the output to eliminate glitches.

Lecture 6: Finite State Machine

Manual design


Example: Synchronous 3-to-9 counter

Lecture 6: Finite State Machine

Manual design

Example: Synchronous 3-to-9 counter

Step 1: State transition diagram

 


Lecture 6: Finite State Machine

Manual design

Example: Synchronous 3-to-9 counter

Step 1: State transition diagram

 

Step 2: Truth table

Truth table for nx_state

pr_state	nx_state
q ₃ q ₂ q ₁ q ₀	d ₃ d ₂ d ₁ d ₀
0 0 1 1	0 1 0 0
0 1 0 0	0 1 0 1
0 1 0 1	0 1 1 0
0 1 1 0	0 1 1 1
0 1 1 1	1 0 0 0
1 0 0 0	1 0 0 1
1 0 0 1	0 0 1 1

Lecture 6: Finite State Machine


Manual design

Example: Synchronous 3-to-9 counter

Step 3: Boolean expressions

Truth table for nx_state

pr_state q ₃ q ₂ q ₁ q ₀	nx_state d ₃ d ₂ d ₁ d ₀
0 0 1 1	0 1 0 0
0 1 0 0	0 1 0 1
0 1 0 1	0 1 1 0
0 1 1 0	0 1 1 1
0 1 1 1	1 0 0 0
1 0 0 0	1 0 0 1
1 0 0 1	0 0 1 1

 

Karnaugh map for d ₃					Karnaugh map for d ₂				
q ₁ q ₀	q ₃ q ₂				q ₁ q ₀	q ₃ q ₂			
	00	01	11	10		00	01	11	10
00	X	0	X	1	00	X	1	X	0
01	X	0	X	0	01	X	1	X	0
11	0	1	X	X	11	1	0	X	X
10	X	0	X	X	10	X	1	X	X

$$d_3 = q_3 \cdot q_0' + q_2 \cdot q_1 \cdot q_0$$

$$d_2 = q_2 \cdot q_1' + q_2 \cdot q_0' + q_2' \cdot q_1$$

$$d_1 = q_1' \cdot q_0 + q_1 \cdot q_0'$$

$$d_0 = q_3 + q_0'$$

Lecture 6: Finite State Machine

Manual design

Example: Synchronous 3-to-9 counter


Step 4: Circuit

$$d_3 = q_3 \cdot q_0' + q_2 \cdot q_1 \cdot q_0$$

$$d_2 = q_2 \cdot q_1' + q_2 \cdot q_0' + q_2' \cdot q_1$$

$$d_1 = q_1' \cdot q_0 + q_1 \cdot q_0'$$



$$d_0 = q_3 + q_0'$$

 


Lecture 6: Finite State Machine

FSM Template

Model subject to glitches:

 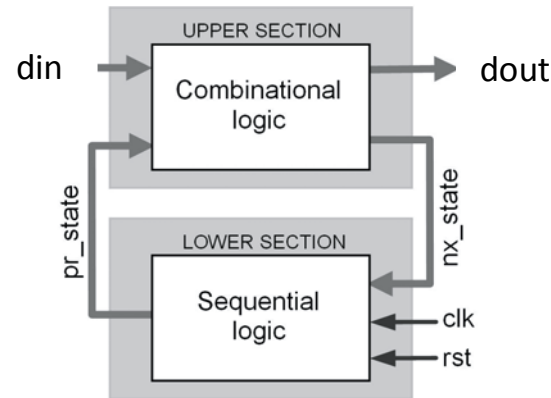

Glitch-free model

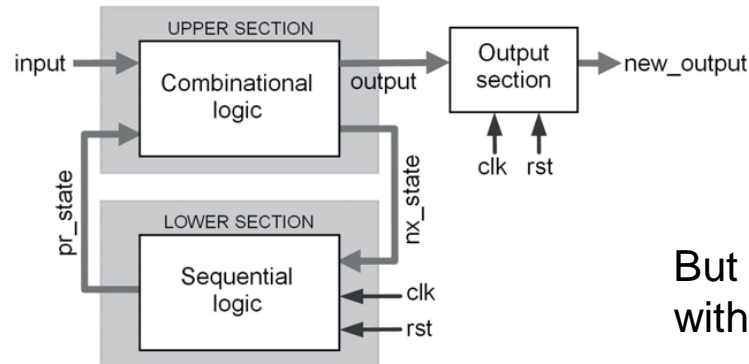

But new_output delayed with respect to output


Lecture 6: Finite State Machine

FSM Template

```
module <entity_name>
  ( input  clk,
    input  rst,
    input  <data_type> din,
    output <data_type> din);
```

```
  typedef enum logic [3:0]{ A = 1, B = 4, C, D, ...} state_t;
  state_t pr_state, nx_state;
```


```
  ...
```

 

Lecture 6: Finite State Machine

FSM Template


```
/*----- Lower Section -----*/  
always_ff @( posedge clk, negedge rst)  
begin  
    if ( !rst )  
        pr_state <= A;  
    else  
        pr_state <= nx_state;  
end  
  
/*...*/
```

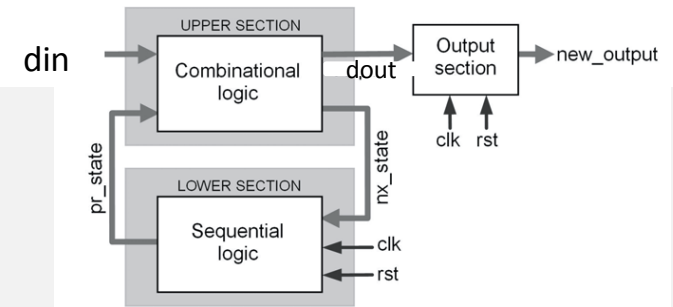

Lecture 6: Finite State Machine

FSM Template

```
/*----- Upper Section -----*/  
always_comb begin  
  
    nx_state = pr_state;  
  
    unique case ( pr_state ) begin  
        A :  
            if( din == <value> )  
                nx_state = B;  
            else  
                nx_state = A;  
        B :  
            if( din == <value> )  
                nx_state = C;  
            else  
                nx_state = A;  
        C : ...  
    end  
end  
/*...*/
```

 


Lecture 6: Finite State Machine

FSM Template

```
/* ----- Output Section ----- */
always_comb begin
    dout = 'b0;
    unique case ( pr_state ) begin
        A : dout = <value>;
        B : dout = <value>;
        C : ...
    end
end

/* ----- Synchronous output ----- */
always_ff @( posedge clk, negedge rst)
begin
    if ( !rst )
        new_output = <value>;
    else
        new_output = dout;
end
endmodule
```

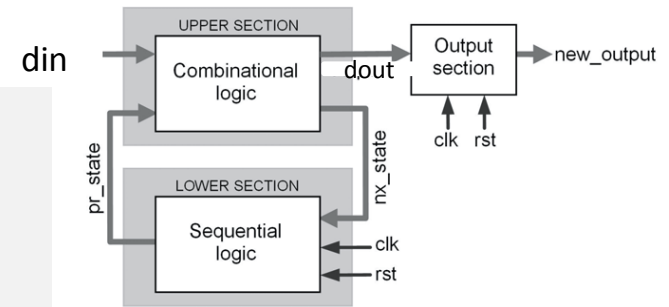


Lecture 6: Finite State Machine

FSM Example #1: BCD Counter

Lecture 6: Finite State Machine

FSM Example #1: BCD Counter

 


Lecture 6: Finite State Machine

FSM Example #1: BCD Counter

```
module counter
( input          clk,
  input          rst,
  output logic [3:0] count
);
typedef enum (zero, one, two, three, four, five, six, seven, eight, nine) state_t;
state_t pr_state, nx_state;

/* ... */
```

 


Lecture 6: Finite State Machine

FSM Example #1: BCD Counter

```
module counter
  ( input      clk,
    input      rst,
    output logic [3:0] count
  );
  typedef enum ( zero, one, two, three, four, five, six, seven, eight, nine ) state_t;
  state_t pr_state, nx_state;

  /* ----- Lower section: ----- */
  always_ff @( posedge clk, negedge rst)
  begin
    if ( !rst )
      pr_state <= zero;
    else
      pr_state <= nx_state;
  end

  /* ... Continue to next page */
```

 

Lecture 6: Finite State Machine

FSM Example #1: BCD Counter

```
/*----- Upper Section -> Next state -----*/
```

```
always_comb begin
```

```
    nx_state = pr_state;
```

```
    unique case ( pr_state ) begin
```

```
        zero : nx_state = one;
```

```
        one  : nx_state = two;
```

```
        two  : nx_state = three;
```

```
        three: nx_state = four;
```

```
        four : nx_state = five;
```

```
        five : nx_state = six;
```

```
        six  : nx_state = seven;
```

```
        seven: nx_state = eight;
```


```
        eight: nx_state = nine;
```

```
        nine : nx_state = zero;
```

```
    end
```

```
end
```

```
/* ... Continue to next page */
```

 

Lecture 6: Finite State Machine

FSM Example #1: BCD Counter

```
/*----- Upper Section -> Output -----*/
```

```
always_comb begin
```

```
    count = 4'b0000;
```

```
    unique case ( pr_state ) begin
```

```
        zero : count = 4'b0000;
```

```
        one  : count = 4'b0001;
```

```
        two  : count = 4'b0010;
```

```
        three: count = 4'b0011;
```

```
        four : count = 4'b0100;
```

```
        five : count = 4'b0101;
```

```
        six  : count = 4'b0110;
```

```
        seven: count = 4'b0111;
```


```
        eight: count = 4'b1000;
```

```
        nine : count = 4'b1001;
```

```
    end
```

```
end
```


```
endmodule
```

 

Lecture 6: Finite State Machine

FSM Example #2

- The system has two states (stateA and stateB), and
- must change from one to the other every time $d = '1'$ is received.
- The desired output is $x = a$ when the machine is in stateA, or $x = b$ when in stateB.
- The initial (reset) state is stateA.

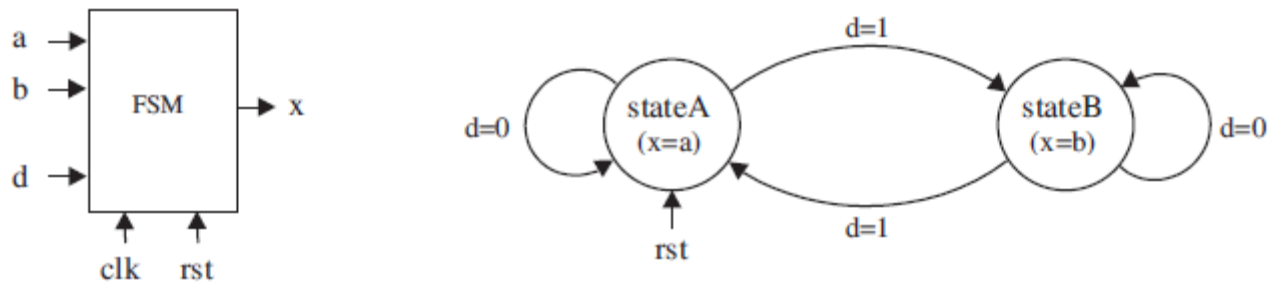


Lecture 6: Finite State Machine

FSM Example #2

```
module simple_fsm
  ( input  clk,
    input  rst,
    input  a,
    input  b,
    input  d,
    output x
  );
  typedef enum ( stateA, stateB ) state_t;
  state_t pr_state, nx_state;

  /* ----- Lower section: ----- */
  always_ff @( posedge clk, negedge rst)
  begin
    if ( !rst )
      pr_state <= stateA;
    else
      pr_state <= nx_state;
  end


  /* ... Continue to next page */
```

 

Lecture 6: Finite State Machine

FSM Example #2

```
/*----- Upper Section -> Next state -----*/
always_comb begin
    nx_state = pr_state;
    unique case ( pr_state ) begin
        stateA :
            if ( d == 1'b1 )
                nx_state = stateB;
            else
                nx_state = stateA;
        stateB :
            if ( d == 1'b1 )
                nx_state = stateA;
            else
                nx_state = stateB;
    end
end
/*----- Upper Section -> Output -----*/
always_comb begin
    x = 1'b0;
    unique case ( pr_state ) begin
        stateA : x = a;
        stateB : x = b;
    end
end
endmodule
```

 

Lecture 6: Finite State Machine

FSM Example #3

- The system has two states (stateA and stateB), and
- must change from one to the other every time $d = '1'$ is received.
- The desired output is $x = a$ when the machine is in stateA, or $x = b$ when in stateB.
- The initial (reset) state is stateA.
- we want the **output to be synchronous** (to change only when clock rises).

Lecture 6: Finite State Machine


FSM Example #3

```
module simple_fsm
  ( input  clk,
    input  rst,
    input  a,
    input  b,
    input  d,
    output x
  );
  typedef enum ( stateA, stateB ) state_t;
  state_t pr_state, nx_state;

  logic local_out;

  /* ----- Lower section: ----- */
  always_ff @( posedge clk, negedge rst)
  begin
    if ( !rst )
      pr_state <= stateA;
      x <= 1'b0;
    else
      pr_state <= nx_state;
      x <= local_out;
    end


  /* ... Continue to next page */
```

 

Lecture 6: Finite State Machine

FSM Example #3


```
/*----- Upper Section -> Next state -----*/
always_comb begin
    nx_state = pr_state;
    unique case ( pr_state ) begin
        stateA :
            if ( d == 1'b1 )
                nx_state = stateB;
            else
                nx_state = stateA;
        stateB :
            if ( d == 1'b1 )
                nx_state = stateA;
            else
                nx_state = stateB;
    end
end
/*----- Upper Section -> Output -----*/
always_comb begin
    x = 1'b0;
    unique case ( pr_state ) begin
        stateA : local_out = a;
        stateB : local_out = b;
    end
end
endmodule
```

 

Lecture 6: Finite State Machine

FSM Example #4: String Detector

- design a circuit that takes as input a serial bit stream and
- outputs a '1' whenever the sequence "111" occurs
- Overlaps must also be considered
 - ✓ 0111110 occurs, then the output remains active for three consecutive clock cycles.

 


Lecture 6: Finite State Machine

FSM Example #4: String Detector

```
module string_detector
( input  clk,
  input  rst,
  input  d,
  input  q
);
  typedef enum ( zero, one, two, three ) state_t;
  state_t pr_state, nx_state;

  /* ----- Lower section: ----- */
  always_ff @( posedge clk, negedge rst)
  begin
    if ( !rst )
      pr_state <= zero;
    else
      pr_state <= nx_state;
  end


  /* Continue to the next page ... */
```

 

Lecture 6: Finite State Machine

FSM Example #4: String Detector

```
/*----- Upper Section -> Next state -----*/
always_comb begin
    nx_state = pr_state;
    unique case ( pr_state ) begin
        zero :
            if ( d == 1'b1 )
                nx_state = one;
            else
                nx_state = zero;
        one :
            if ( d == 1'b1 )
                nx_state = two;
            else
                nx_state = zero;
        two :
            if ( d == 1'b1 )
                nx_state = three;
            else
                nx_state = zero;
        three:
            if ( d == 1'b1 )
                nx_state = zero;
            else
                nx_state = three;
    end
end
/* Continue to the next page ... */
```

 


Lecture 6: Finite State Machine

FSM Example #4: String Detector

```
/*----- Upper Section -> Output -----*/
always_comb begin

    q = 1'b0;


    unique case ( pr_state ) begin
        zero : q = 1'b0;
        one  : q = 1'b0;
        two  : q = 1'b0;
        three: q = 1'b1;
    end
end
endmodule
```

 

Lecture 6: Finite State Machine

FSM Exercise : Traffic Light Controller

- Three modes of operation: Regular, Test, and Standby.
- Regular mode: four states, each with an independent, programmable time, passed to the circuit by means of a parameter.
- Test mode: allows all pre-programmed times to be overwritten (by a manual switch) with a small value, such that the system can be easily tested during maintenance (1 second per state). This value should also be programmable and passed to the circuit using a parameter.
- Standby mode: if set (by a sensor accusing malfunctioning, for example, or a manual switch) the system should activate the yellow lights in both directions and remain so while the standby signal is active.
- Assume that a 60 Hz clock (obtained from the power line itself) is available.

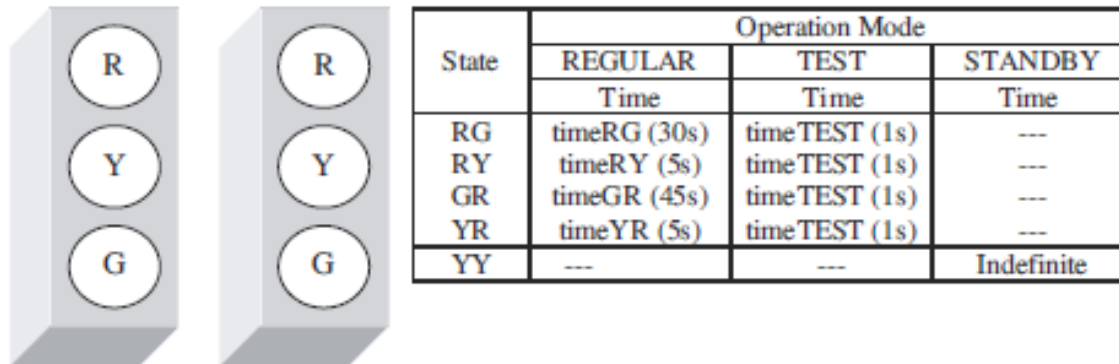

Lecture 6: Encoding Styles

- Sequential (*)
- Gray
- Johnson
- One-hot
- User-defined

Lecture 6: Encoding Styles


- Gray
 - Two successive values differ in only one bit

Decimal	Gray	Binary
0	000	000
1	001	001
2	011	010
3	010	011
4	110	100
5	111	101
6	101	110
7	100	111

Lecture 6: Encoding Styles

- Gray
 - Two successive values differ in only one bit

Decimal	Gray	Binary
0	000	000
1	001	001
2	011	010
3	010	011
4	110	100
5	111	101
6	101	110
7	100	111

 

Lecture 6: Encoding Styles

- Johnson
 - It is created using a simple rotation, the rotating bit is **inverted**.

Johnson

000

100

110

111

011

001

Lecture 6: Encoding Styles

- Johnson
 - It is created using a simple rotation, the rotating bit is **inverted**.

Johnson

000


100

110

111

011

001

 

Lecture 6: Encoding Styles


- One-hot
 - Only a single bit is high ('1') and all others are low ('0')

Binary	One-hot
000	00000001
001	00000010
010	00000100
011	00001000
100	00010000
101	00100000
110	01000000
111	10000000

Lecture 6: Encoding Styles

- One-hot
 - Only a single bit is high ('1') and all others are low ('0')

Binary	One-hot
000	00000000 1
001	0000000 1 0
010	00000 1 00
011	0000 1 000
100	000 1 0000
101	00 1 00000
110	0 1 000000
111	1 0000000

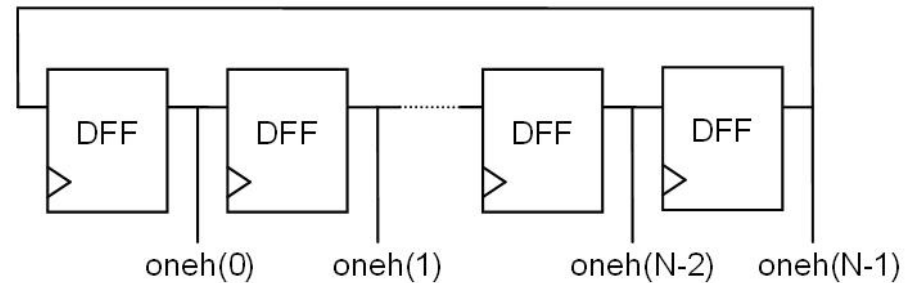

Lecture 6: Encoding Styles

- How many states can be encoded with $N=4$ flip-flops using:
 - Sequential

Lecture 6: Encoding Styles

- How many states can be encoded with $N=4$ flipflops using:
 - Sequential $= 16 = 2^N$
 - Gray

Lecture 6: Encoding Styles

- How many states can be encoded with $N=4$ flipflops using:
 - Sequential $= 16 = 2^N$
 - Gray $= 16 = 2^N$
 - Johnson

Lecture 6: Encoding Styles

- How many states can be encoded with $N=4$ flipflops using:
 - Sequential $= 16 = 2^N$
 - Gray $= 16 = 2^N$
 - Johnson $= 8 = 2^{*N}$
 - One-hot

Lecture 6: Encoding Styles

- How many states can be encoded with $N=4$ flipflops using:
 - Sequential $= 16 = 2^N$
 - Gray $= 16 = 2^N$
 - Johnson $= 8 = 2 \cdot N$
 - One-hot $= 4 = N$

Lecture 6: Encoding Styles

- When to use Which
Sequential (or Gray) code?

Lecture 6: Encoding Styles

- When to use Which

Sequential (or Gray) code?

Least number of flip-flops, but largest combinational logic
(slowest)

One-hot code?

Lecture 6: Encoding Styles

- When to use Which

Sequential (or Gray) code?

Least number of flip-flops, but largest combinational logic
(slowest)

One-hot code?

Largest number of flip-flops, but smallest combinational logic
(fastest)

Johnson code?

In between